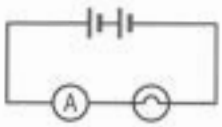
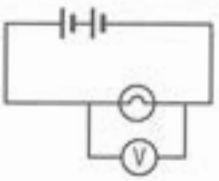
Ammeters and voltmeters 6a

Ammeters	Voltmeters
	
■ Used to measure current (number of moving electrons) through an appliance.	■ Used to measure potential difference (the amount of electrical potential or pressure between two points).
■ Current is measured in amperes. (1 ampere means that 6 300 000 000 000 000 000 electrons pass by every second.)	■ Potential difference is measured in volts.
■ Low resistance to electricity and should not be connected straight across the power supply.	■ High resistance to electricity and able to be connected straight across the power supply.
■ Large amounts of current pass through.	■ Tiny amounts of current pass through.
■ Electric current is the same everywhere in a series circuit.	■ Potential difference varies for different appliances.
■ Energy is used up by the lamp.	■ Energy is used up around the circuit.
■ Connected in series next to the appliance.	■ Placed in parallel across the appliance.

1 The table provides summary notes about ammeters and voltmeters. Write the corresponding points into contrasting sentences using connectives such as: *but, and, on the other hand, while.* The first one has been done for you.

a Ammeters are used to measure current through an appliance, whereas voltmeters measure the difference in electrical potential between two points.

b _____

_____

c _____

_____

d _____

_____

e _____

_____

f _____

_____

g _____

_____


© Suada Bilali, Chris Greef and Learning Essentials, 2003.


Ammeters and voltmeters 6b


2 For each of the diagrams add and draw:


a an ammeter to measure the current through the light globes and

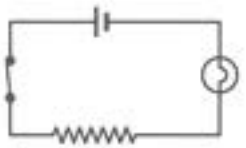b a voltmeter to measure the potential difference across the resistors.



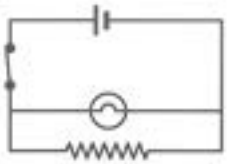

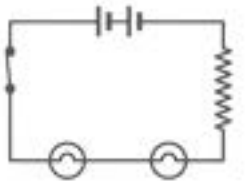

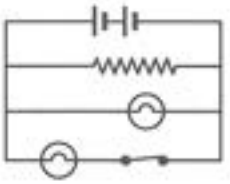


3 Jill set up the following circuit in Ms Smart's classroom, but only recorded three measurements and forgot to label some of the measuring devices. Look at the diagram and answer the questions.

a What sort of measuring devices are the following?

i) _____

ii) _____

iii) _____

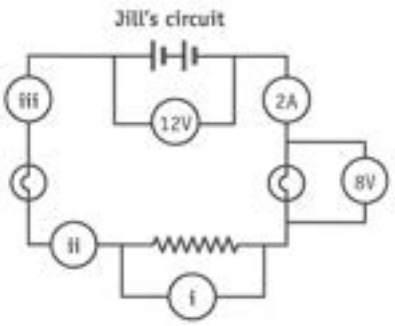


b What is the reading on the meters?


i) _____


ii) _____

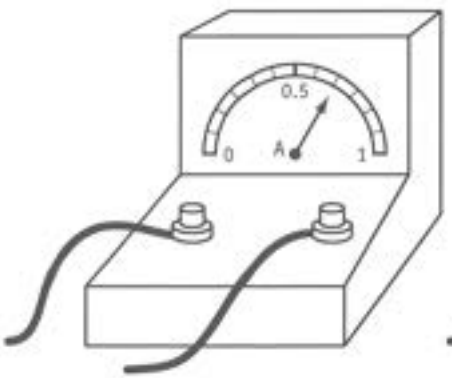iii) _____

4 Write down the readings depicted on the following ammeters.



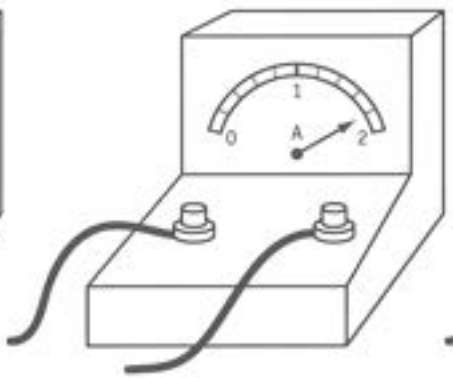

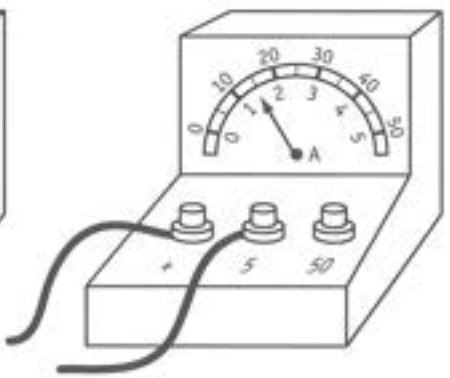

a _____ b _____ c _____

© Suada Bilali, Chris Greef and Learning Essentials, 2003.