Changing circuits

8

Look at the diagrams below. What would happen if the electric circuit was changed as indicated? Write your predictions in the spaces provided.

1

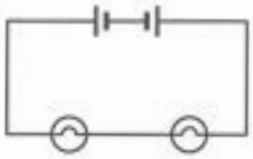

You connect the batteries this way.

2

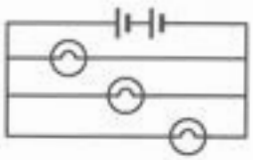

You add another globe.

3

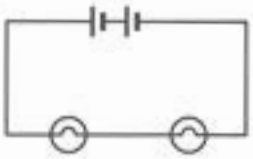

You loosen one globe.

4

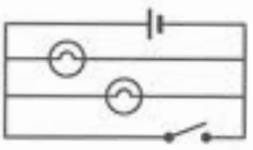

You press on the switch.

5

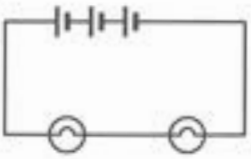

You add another battery.

6

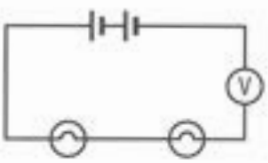

You add this voltmeter to the circuit.

7

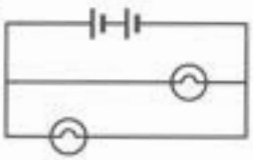

You unscrew one globe.

8

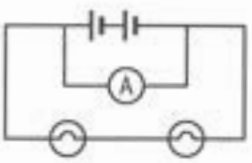

You add this ammeter to the circuit.

9

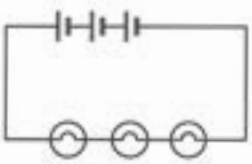

You add another globe.

10

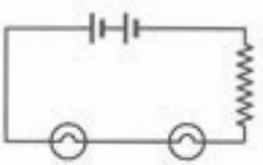

You add a resistor to the circuit.

© Suada Bilali, Chris Greef and Learning Essentials, 2003.