Task

Choose one task from each column.

The more challenging tasks have more stars. Collect as many stars as you can.

Write an A-Z on electricity and circuits. ★	Write lyrics to the chorus of "Let it go", explaining how current flows in an series circuit. ★★	In a series circuit, which of these is the most important and why – wires, battery or light bulb? ★★
Draw three different series circuits. ★	Plan an experiment to test the current at different parts of a series circuit. Include a circuit diagram to help explain. ★★★	Draw a logo to describe current. ★★
Draw a table showing the circuit symbols and the names of five different components. ★	Explain the difference between current and voltage in series circuits in exactly 48 words. ★★	Trace the outline of your hand. On each finger write a fact about series circuits, current or voltage. On the palm write some keywords. ★
	Create a superhero that has powers related to current and voltage. Produce a fully annotated drawing. ★★★	Draw a diagram of a series circuit that won't work. Explain how to fix the circuit and what is wrong with it. ★★



Keywords

circuit
ammeter
voltmeter
power pack
current
charge
electrons
copper wire
conductor
amps

volts