Questions

1. What EC is the flow of charge?
2. Which I doesn't let charge flow through it?
3. Which A is used to measure current?
4. Which P is a type of circuit?
5. Which S has to be closed to complete a circuit?
6. Which M conducts electricity?
7. Which E's move through a circuit?
8. Which PD is measured by a voltmeter?
9. Which O is the unit for resistance?
10. Which V must be placed in parallel around the component it is testing?
11. What FL's are wired in series?
12. Which B supplies a direct current?
13. What does AC stand for?
14. Which B is the colour of the live wire in a plug?
15. Which B is the colour of a neutral wire in a plug?
16. Which H is the unit for frequency?
17. Which P is current X voltage?
18. As the temperature of a filament lamp increases which R also increase?

Answers

1. electric current
2. insulator
3. ammeter
4. parallel
5. switch
6. metal
7. electrons
8. potential difference
9. ohm
10. voltmeter
11. fairy lights
12. battery
13. alternating current
14. brown
15. blue
16. hertz
17. power
18. resistance

© www.teachitscience.co.uk 2014