

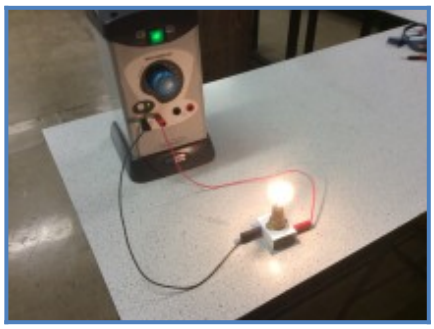


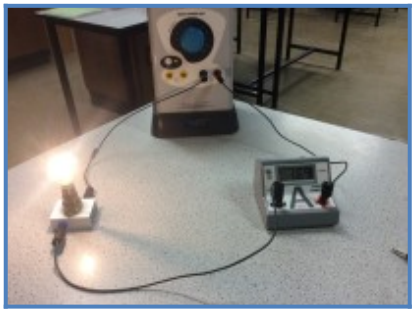This is a simple series circuit.
Draw the circuit diagram in the
box opposite.



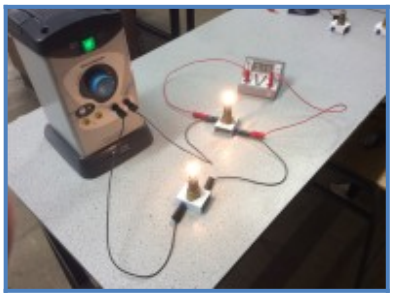This circuit shows three pieces of equipment. Draw a circuit diagram and label each piece of equipment.



Draw this circuit diagram in the box opposite. Label each piece of equipment.

Keywords

amps
ammeter

bulb

charge
conductor
copper
current

charge

insulator

power pack
potential difference (voltage)


voltmeter
volts


wire


What is the rule for placing an ammeter in a circuit and what does it measure?


What is the rule for placing a voltmeter in a circuit and what does it measure?


Answers

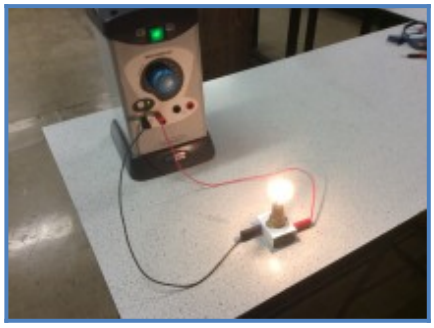


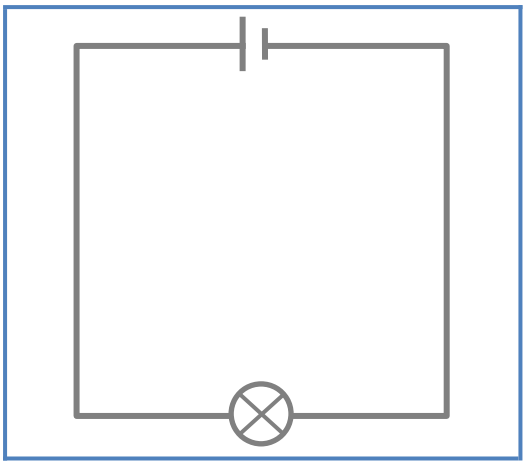

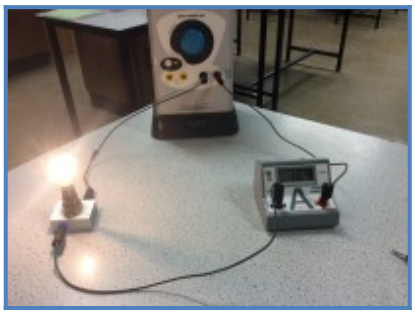

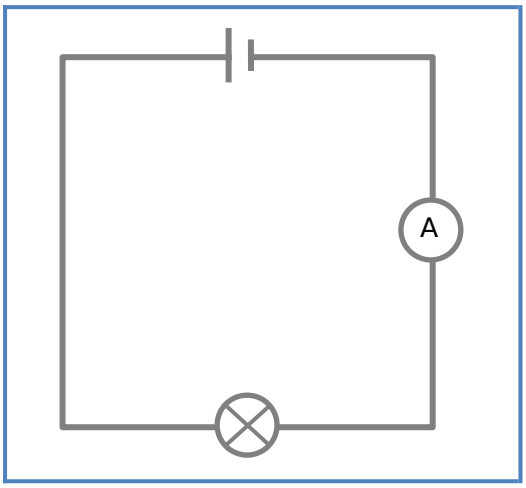

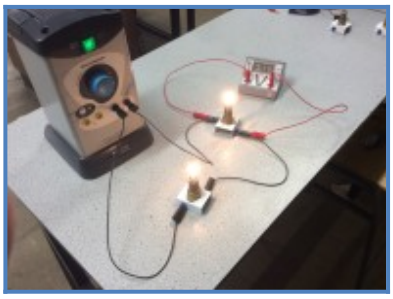

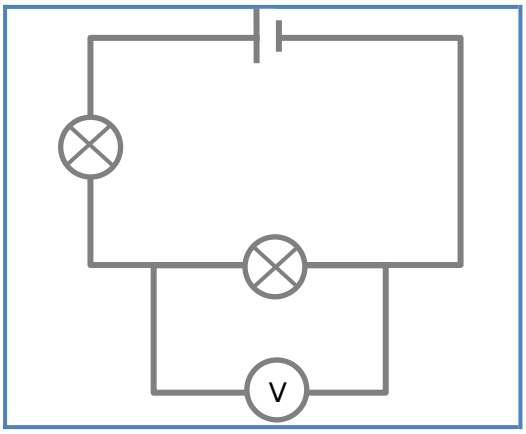

What is the rule for placing an ammeter in a circuit and what does it measure?
The ammeter measures current. It is placed in series
What is the rule for placing a voltmeter in a circuit and what does it measure?
The voltmeter measures potential difference across a component. It is placed in parallel to the component that you want to measure.