Resistance and Power Name _____


1. Match up terms with definitions by writing the correct letter of each definition in the box beside each term.

Definition

a. A complete conducting pathway
b. Meter used to measure the size of a current
c. Negatively charged particles which are parts of atoms
d. Energy which is stored in objects
e. Current which travels in one direction only
f. Object which has an excess or deficiency of electrons
g. Objects which are part of electrical circuits
h. Circuit in which there are two or more pathways
i. The flow of electrons around a conducting pathway
j. Unit of voltage gain or loss
k. Object which converts electrical energy into other forms
l. Particles that all matter is made of
m. Electrons which are able to travel through a substance
n. Point of attachment for wires to a battery or meter
o. Meter used to measure the gain or loss of voltage
p. Unit of current
q. An object such as a battery or a dynamo
r. Current which keeps changing direction
s. Circuit in which all components are in a single loop
t. Created by the difference in charge between locations
u. The loss or gain of energy by the current

Terms

	Attempt	
	1st	2nd
Electrons		
Atoms		
Charged		
Terminal		
Potential energy		
Electrical force field		
Current		
Free electrons		
Circuit		
Energy supplier		
Components		
Energy user		
Series circuit		
Parallel circuit		
Ammeter		
Ampere or amp		
Direct current		
Alternating current		
Voltage gain or loss		
Volt		
Voltmeter		

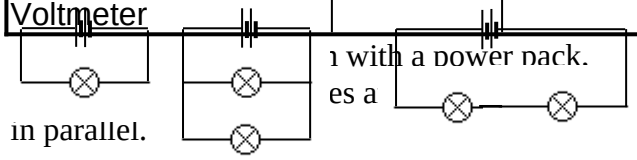

ı with a power pack.
es a

ın parallel.

3. Complete.

In a series circuit, the _____is the same at all points. When batteries are connected in series the voltages are _____ together. When lamps are connected in series, the voltage gained from the _____ is shared between them so the bulbs will be _____.

In a parallel circuit, the _____ of the currents in the branches is equal to the total _____ flowing in the circuit. When lamps are connected in parallel each bulb receives the full _____ supplied to the current by the batteries, so the bulbs will be _____.

4. The lamps are all of equal strength and the cells are all 1.5V.

Circuit A Circuit B Circuit C

a. How many volts will the current in each circuit receive? _____

b. In which circuit will the bulbs be brightest? __

c. In which circuit will the bulbs be dimmest? __