LIGHT CIRCUIT

Method: Connect the alligator clips to the ends of the wires and attach one alligator clip to the positive terminal and the other to the negative terminal.

1. Draw a diagram and label the different parts

2. Write the different types of energy each part has

Battery:

Wire:

Light globe:

3. Write a flow diagram to show the transfer of energy.

➔ ➔