Fuses

A fuse is a safety device

It protects a circuit when there is something wrong with the circuit

A short circuit can cause a fire if the fuse does not operate.

Fuses are made of low melting point metals.

In modern houses fuses have been replaced by circuit breakers.

Fuses are used in houses, cars and electrical appliances.

Questions

1. What metal is a fuse made of ?

2. Why is the fuse wire thin

3. How does a fuse stop the electricity flowing when there is something wrong ?

4. How does a circuit breaker stop the electricity flowing when there is something wrong ?

5. Why does the fuse need to have a low melting point

6. Draw the symbol for a fuse

7. Draw a circuit diagram to show how a fuse would be placed in a circuit containing 2 globes, 1 switch and 1 cell

8. Draw a circuit diagram to show how a fuse would be placed in a circuit containing 2 globes in parallel, 1 switch and 1 cell