

Voltage in Series and Parallel Circuits

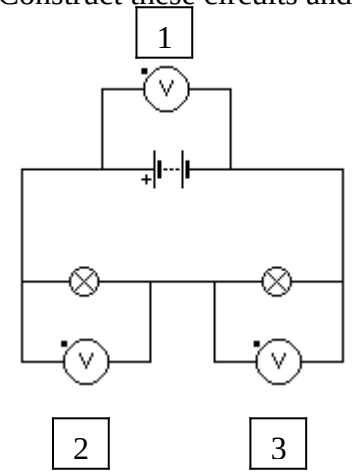Construct these circuits and measure the voltage for each ammeter.



Voltmeter	Voltage (V)
1	
2	
3	

In a series circuit the voltage

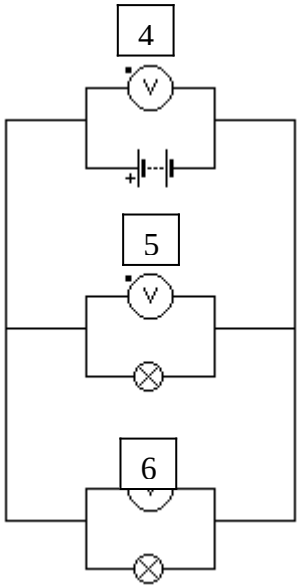


Voltmeter	Voltage (V)
4	
5	
6	

In a parallel circuit the voltage


Voltage in Series and Parallel Circuits

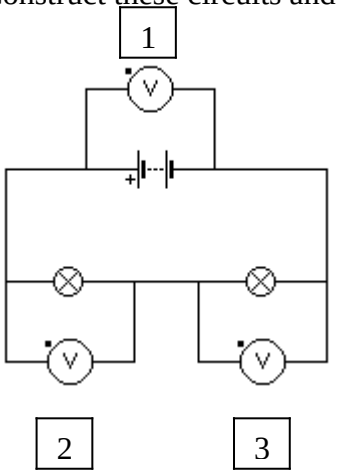Construct these circuits and measure the voltage for each ammeter.



Voltmeter	Voltage (V)
1	
2	
3	

In a series circuit the voltage

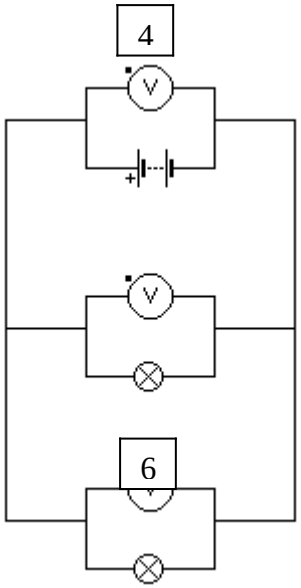

Voltmeter	Voltage (V)
4	
5	
6	

In a parallel circuit the voltage