Batteries and Cells

A cell is a device which converts chemical energy into electrical energy.

It is used in an electrical circuit to drive motors, lights etc.

A battery is a combination of cells.

The cells are connected in either series or parallel to provide higher voltage or longer life.

When connecting cells in series, connect them positive to negative.

Electrical circuits

An electrical circuit allows electrons to flow from the source, through conductors and return to the source.

When they flow through an appliance energy is transferred to the appliance and it works. ie a light glows or a motor runs.

The electrons will not flow unless the circuit is complete.

Circuits can be represented by circuit diagrams.

Symbols represent the various parts of the circuit.