
Circuit diagrams

1

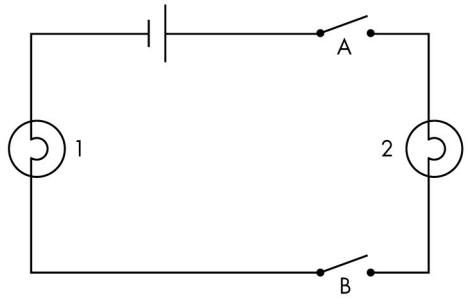

Explain what will happen to globes 1 and 2 when

a both switches are open

_____

b both switches are closed

_____


c switch A is open and switch B is closed

_____

d switch B is open and switch A is closed

_____

2

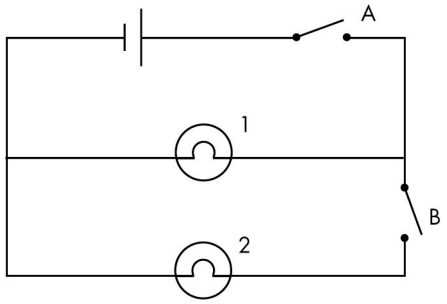

Explain what will happen to globes 1 and 2 when

a both switches are open

_____

b both switches are closed

_____

c switch A is open and switch B is closed


_____

d switch B is open and switch A is closed

_____


Copyright © Pearson Australia (a division of Pearson Australia Group Pty Ltd) – Science Worksheet Searcher

3

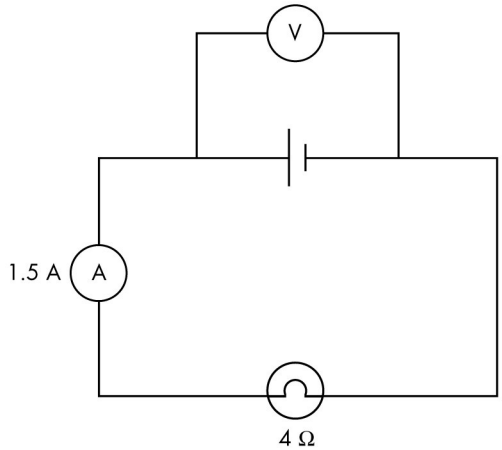


Calculate the voltage across the battery.

4

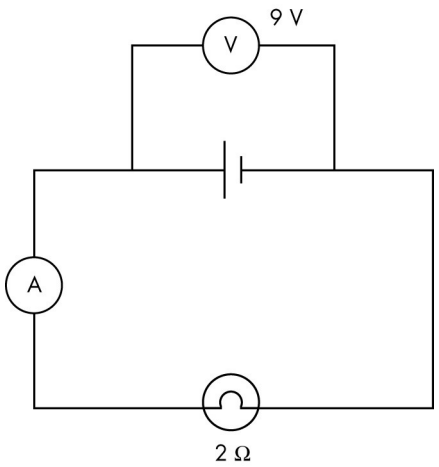


Calculate the current flowing through the ammeter.

5

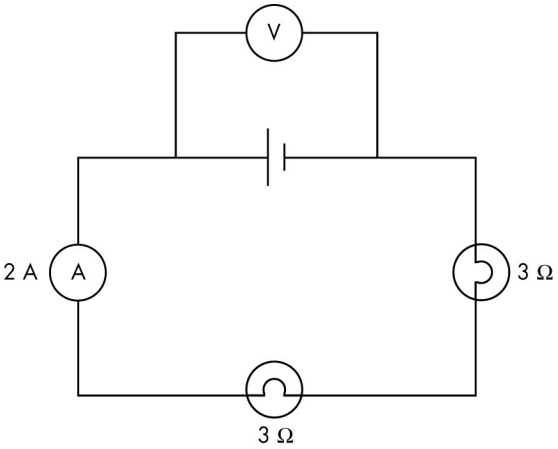

Calculate the voltage across the battery.

6

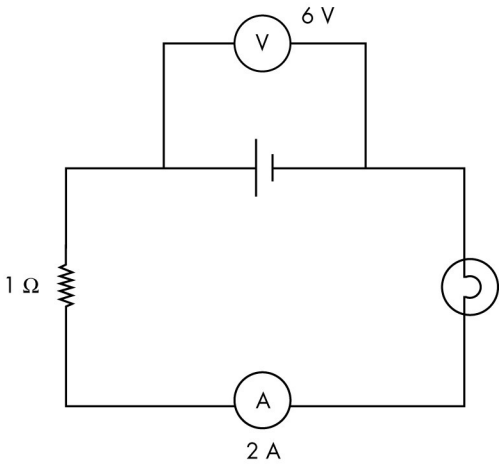

Calculate the resistance of the globe.

Copyright © Pearson Australia (a division of Pearson Australia Group Pty Ltd) – Science Worksheet Searcher