
Completing the circuit

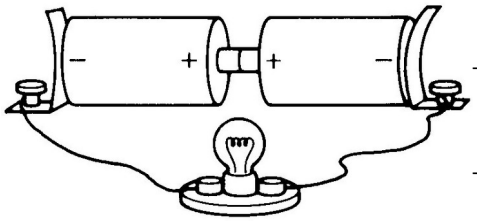
Questions

1 Why don't the bulbs light up in the circuits below?




_____

_____

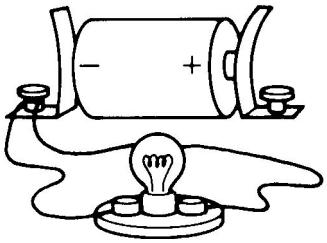

_____


_____

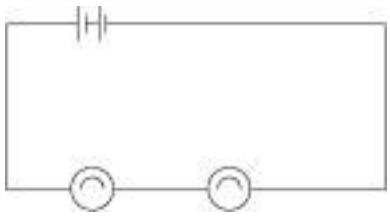


_____

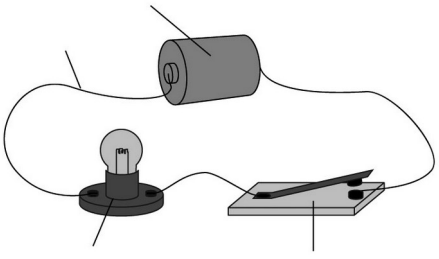_____

2 Label each diagram with the words in the box. Consult your textbook if necessary.




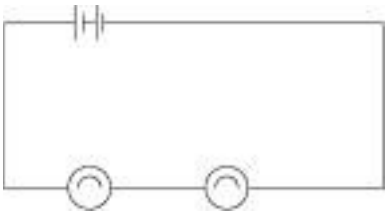


switch
globe
wire
battery

Copyright © Pearson Australia (a division of Pearson Australia Group Pty Ltd) – Science Worksheet Searcher

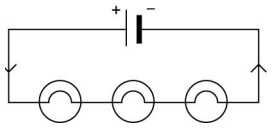
3 Which types of circuits are shown below—a series circuit, a parallel circuit or a combination of both? Write the name beside each circuit diagram.




.....

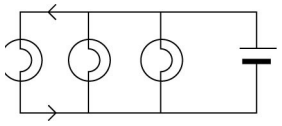

.....

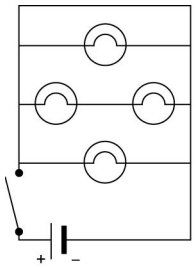


.....

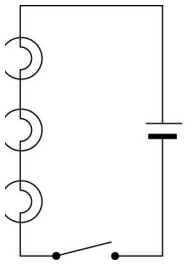


.....

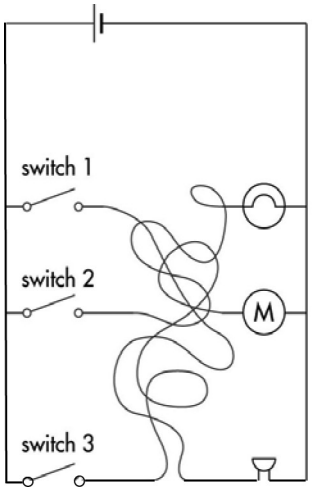4 Look at the diagram below, in which the wires are rather tangled. Trace the path of each circuit, and say what will happen when each switch is closed.



Circuit symbols

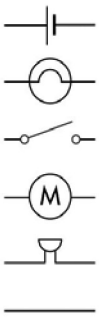

a switch 1 _____

b switch 2 _____

c switch 3 _____

Copyright © Pearson Australia (a division of Pearson Australia Group Pty Ltd) – Science Worksheet Searcher