
CIRCUIT SYMBOLS

Circuit diagrams make it easier to assemble and understand how circuits work.

The following symbols need to be memorised.

Notice that some components have two possible symbols - ***either is acceptable***.

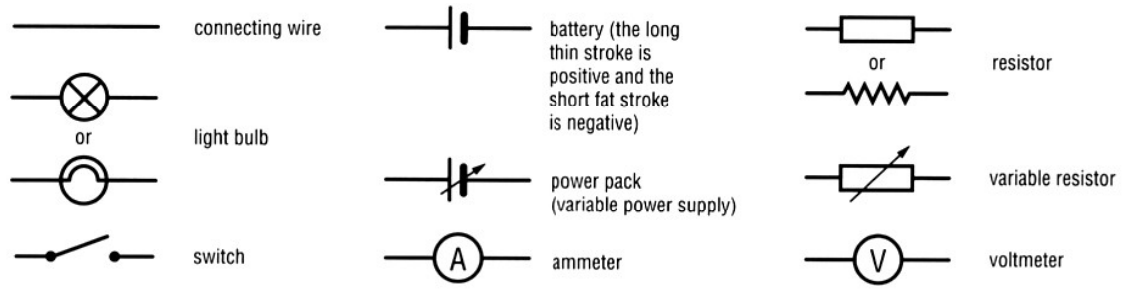e.g. Look at light globes, resistors and variable resistors.



Below are two examples of drawing simple circuits.

