Set up these two circuits and complete the statement.

Two identical lamps will glow brighter in a _____ circuit than in a _____ circuit.

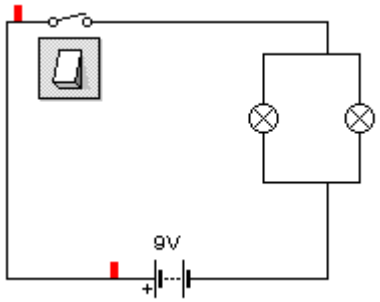

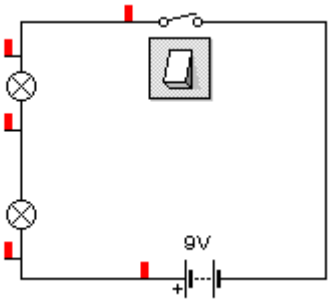

Set up these two circuits and complete the statement.

Two identical lamps will glow brighter in a _____ circuit than in a _____ circuit.

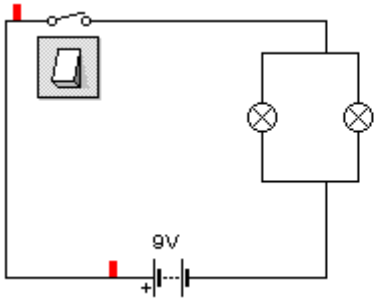

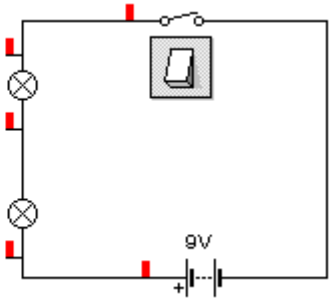

Set up these two circuits and complete the statement.

Two identical lamps will glow brighter in a _____ circuit than in a _____ circuit.

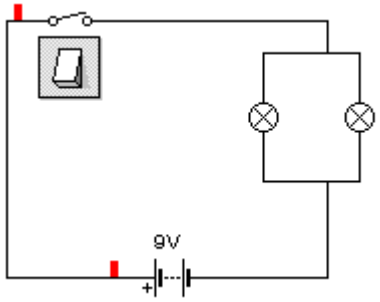

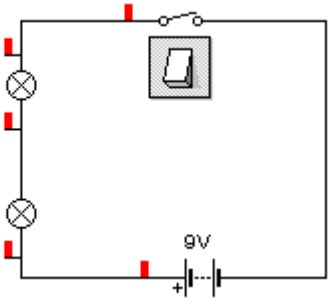

Set up these two circuits and complete the statement.

Two identical lamps will glow brighter in a _____ circuit than in a _____ circuit.

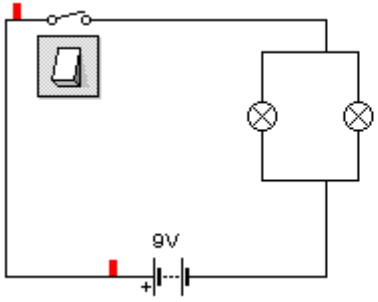

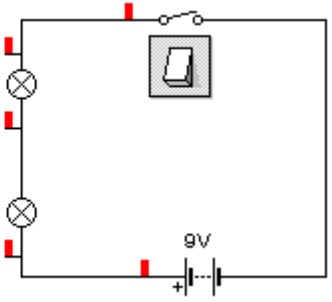

CHALLENGE

Set up a circuit which allows two switches at either end of a hallway to turn the same light on and off.