Current and Circuits

Current electricity is where e_____ are able to flow through a conductor.

Conductors are

_____

_____

And electric circuit is a pathway around which electrons can _____.

Voltage is the electrical _____that pushes electrons around a circuit. Voltage is measured in _____(V).

Current is the _____ which electrons flow through a circuit. Current is measured in _____ (A).

Resistance is measure of how much the current is slowed down while moving through a conductor. Resistance is measured in ohms (____).

Set up the following circuit.

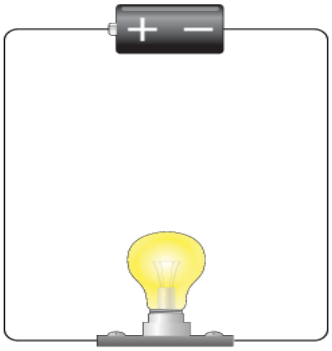

Start with the power pack set at 2 volts. Increase the voltage. What happens to the brightness of the globe?

Set the power pack back to 2 volts. Now add a second globe to the circuit. What happens to the brightness of the globe?