Set up these circuits and compare the brightness of the each lamp with lamp A.
Use the code **B** = **brighter**, **D** = **dimmer**, or **S** = **same brightness**.

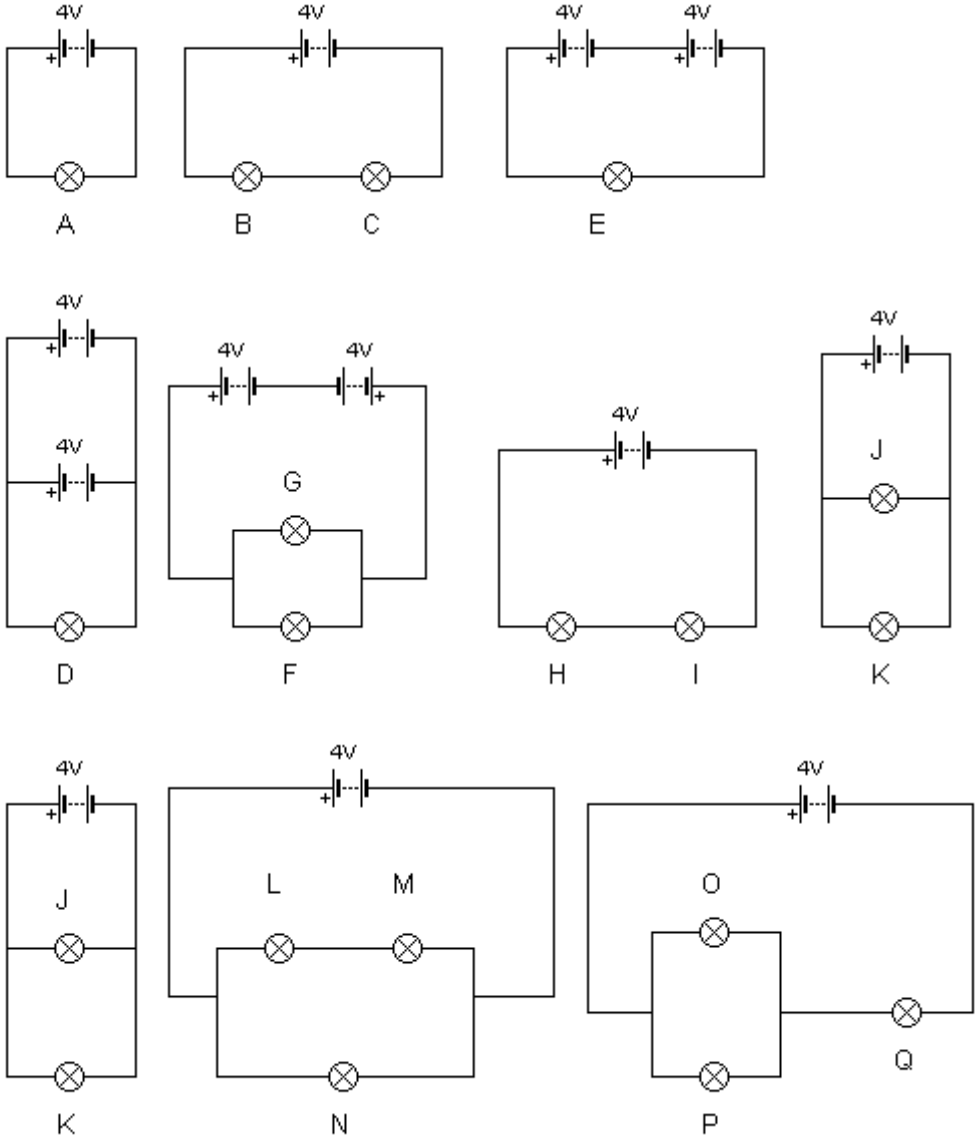

A =	B =	C =	D =	E =	F =
G =	H =	I =	J =	K =	L =
M =	N =	O =	P =	Q =	

Set up these circuits and compare the brightness of the each lamp with lamp A.
Use the code **B** = **brighter**, **D** = **dimmer**, or **S** = **same brightness**.

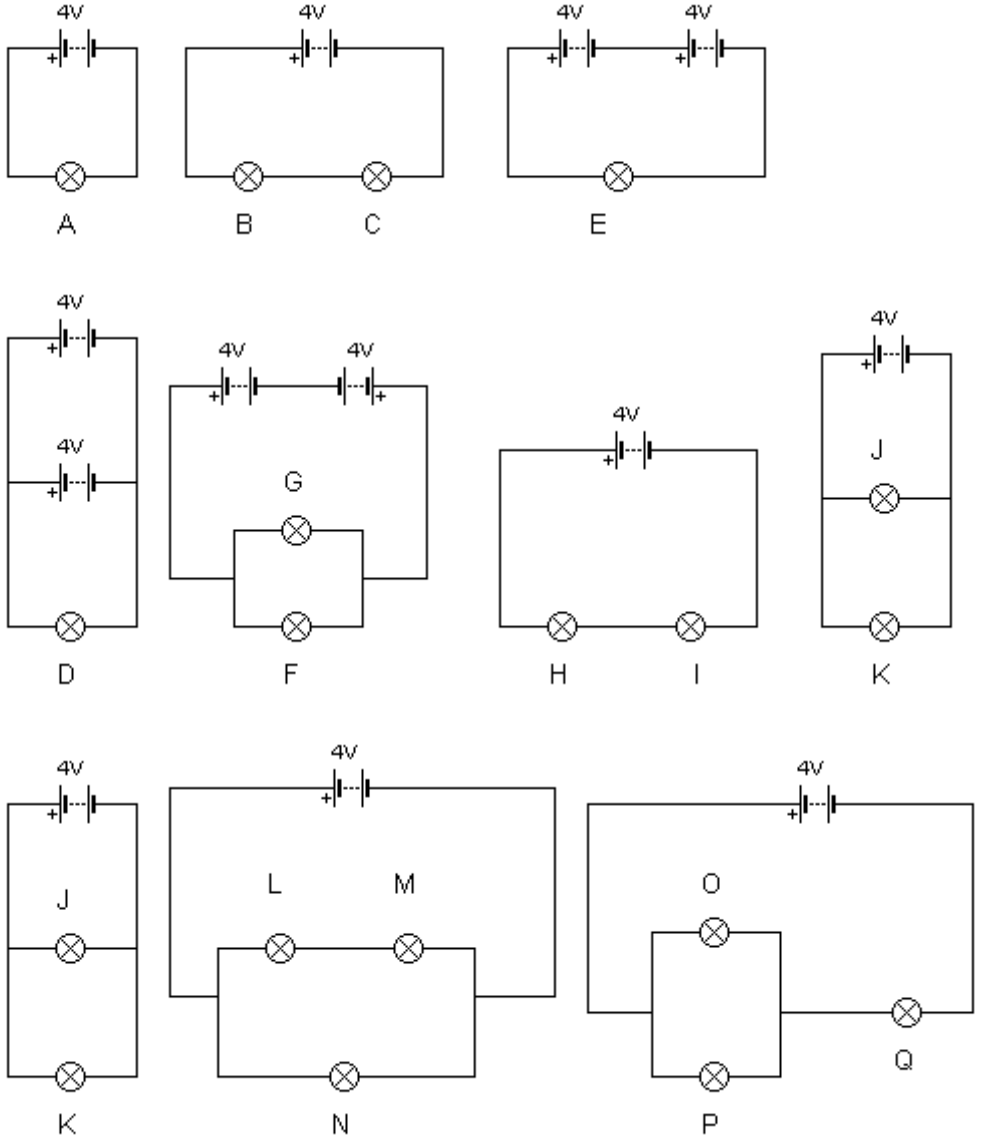

A =	B =	C =	D =	E =	F =
G =	H =	I =	J =	K =	L =
M =	N =	O =	P =	Q =	