Current in Series and Parallel Circuits

Construct these circuits and measure the current for each ammeter.

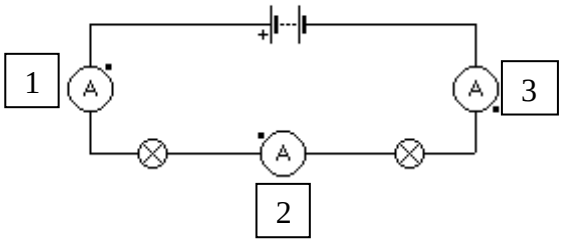

Ammeter	Current (A)
1	
2	
3	

In a series circuit the current

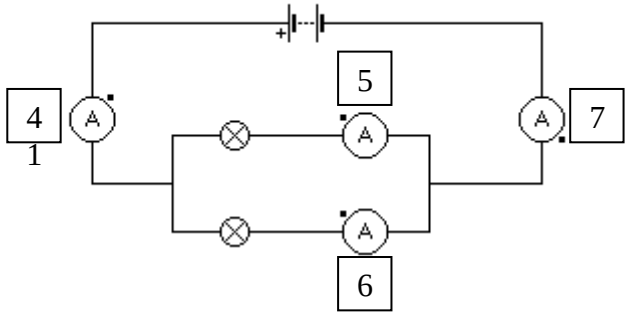

Ammeter	Current (A)
4	
5	
6	
7	

In a parallel circuit the current

Current in Series and Parallel Circuits

Construct these circuits and measure the current for each ammeter.

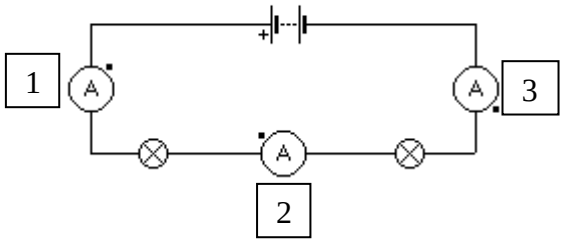

Ammeter	Current (A)
1	
2	
3	

In a series circuit the current

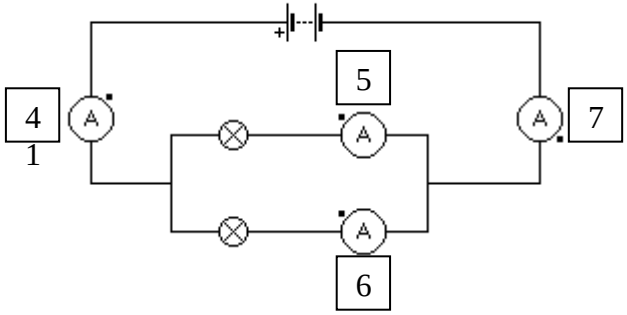

Ammeter	Current (A)
4	
5	
6	
7	

In a parallel circuit the current