Set up these circuits and compare the brightness of the each lamp with lamp A.
Use the code **B** = **brighter**, **D** = **dimmer**, or **S** = **same brightness**.

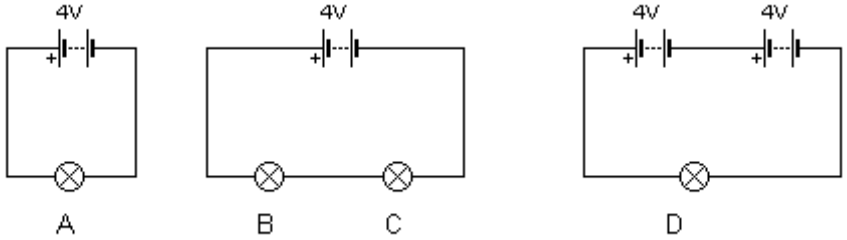

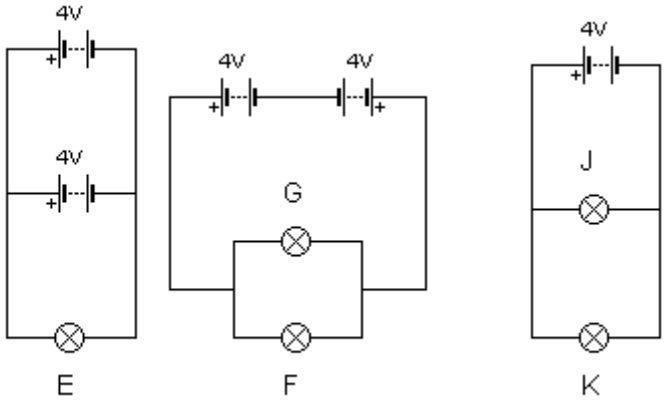

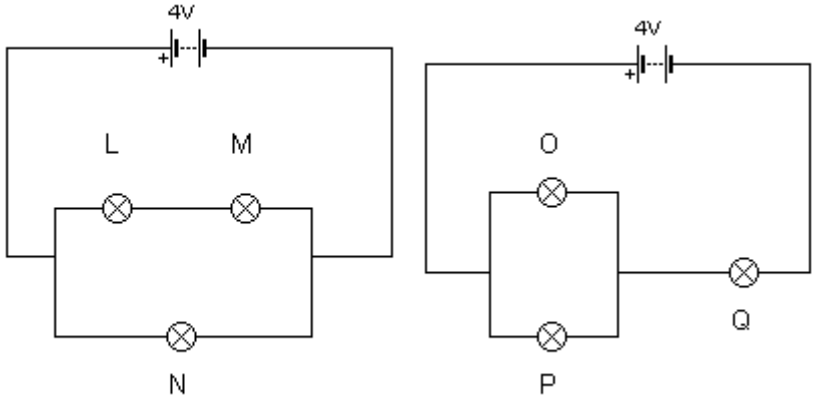

B = D	C = D	D = B	E = S	F = D
G = D	J = S	K = S	L = D	
M = D	N = S	O = D	P = D	Q = D